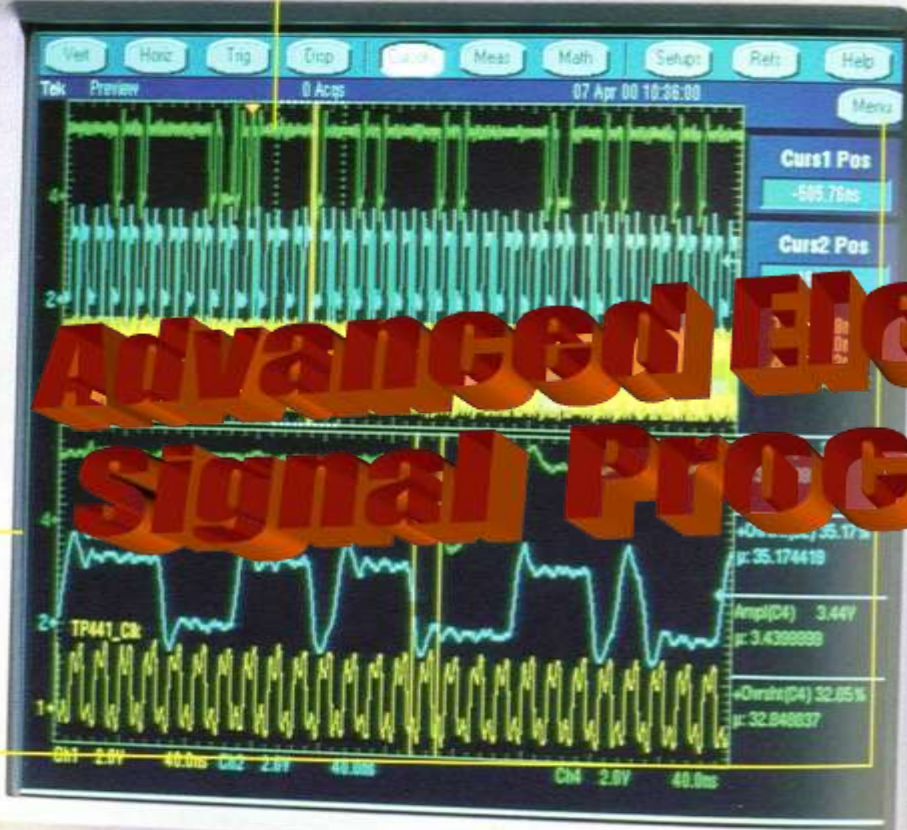


Tektronix TDS 7404 Digital Phosphor Oscilloscope

4 GHz 20 GS/s DPO



# Advanced Electronic Signal Processing

The physical control panel of the oscilloscope features several sections of controls:

- HORIZONTAL POSITION:** Includes knobs for POSITION, DELAY, and RESOLUTION.
- TRIGGER:** Includes buttons for EDGE, ADVANCED, and RUN/STOP.
- VERTICAL:** Includes knobs for POSITION and SCALE for channels CH1, CH2, CH3, and CH4.
- Other Controls:** Includes buttons for FINE, AUTOSET, RESULT, PRINT, and a LEVEL knob.



The bottom panel of the oscilloscope includes several ports and controls:

- PROBE COMPENSATION: SIGNAL, GND, ADJUST, and PROBE AT TIME.
- AUX IN, AUX OUT, and SIGNAL OUT ports.
- Two BNC connectors with cables plugged in.
- A Tektronix TCA-558A module.



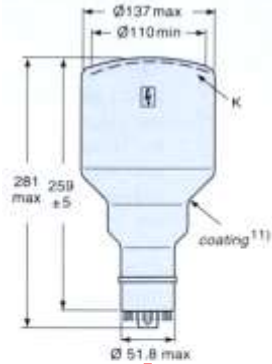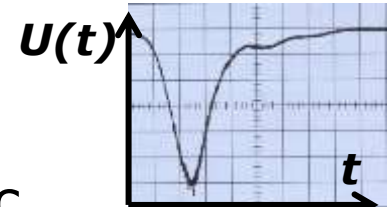
# PM Operation


Fast PM: pulse rise time  $\sim 2\text{ns}$ , gain:  $3 \cdot 10^7$



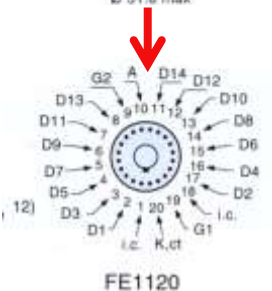
Philips XP2041  
5" dia cathode  
14 dynodes  
+ focussing electrodes




Socket FE1120  
pin connections

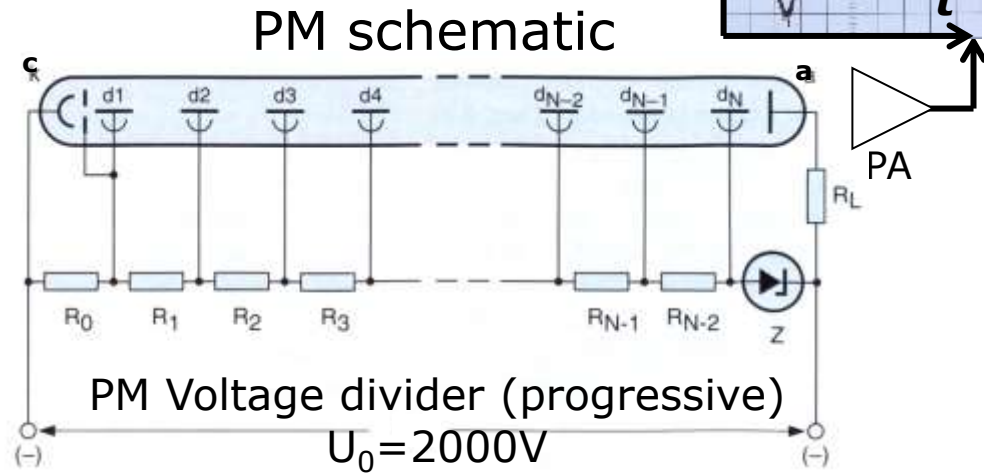


Sockets

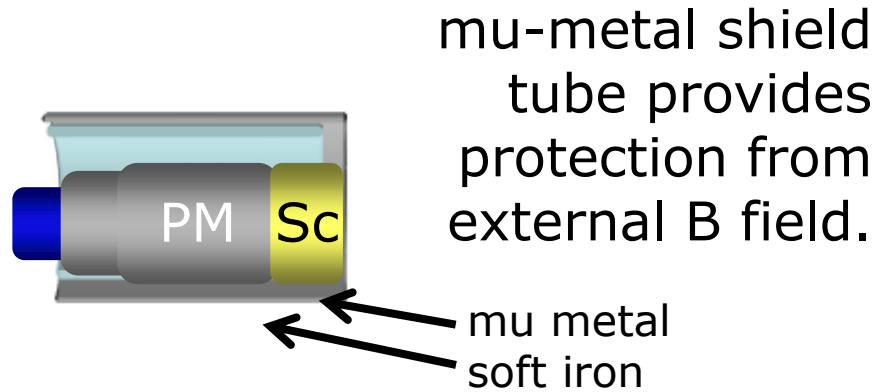

# Basic Counting System

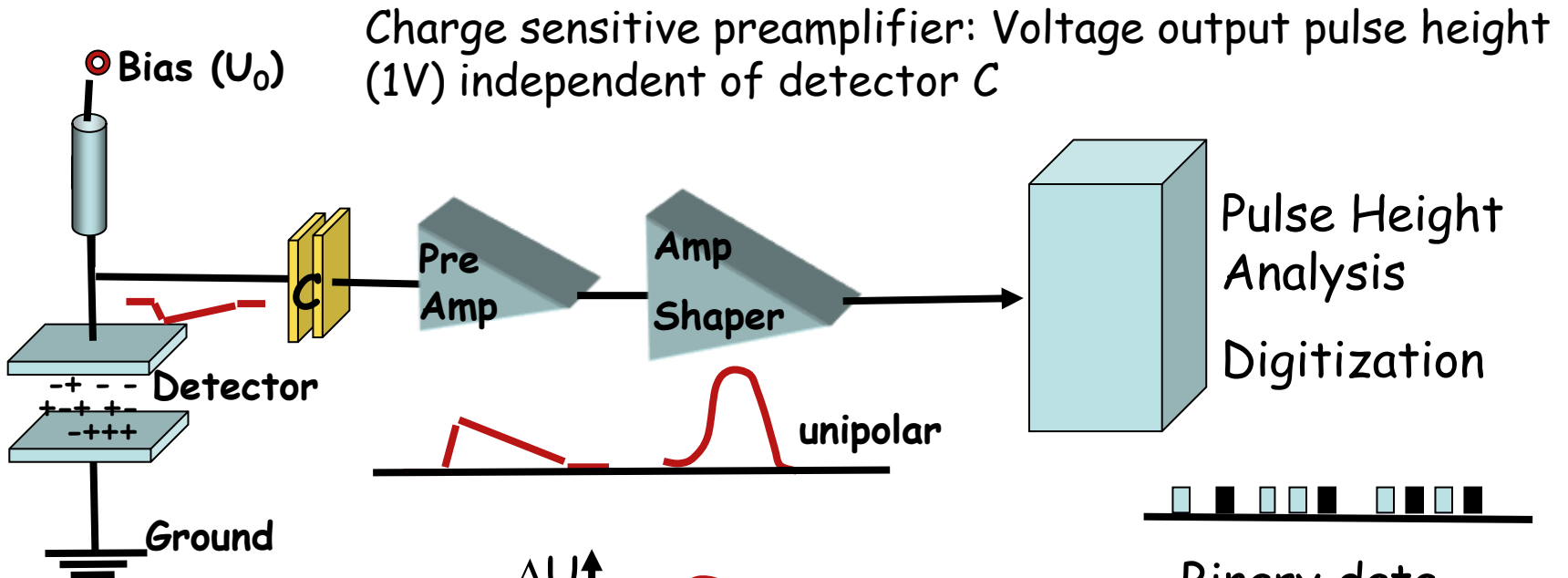

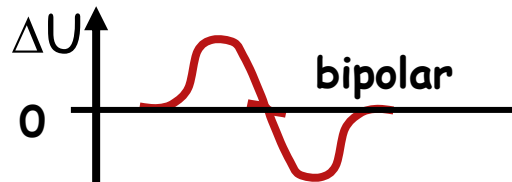R: Load resistor  
C: Insulate electronics from high voltage (bias)  
Pulse height 100 mV





Amplifier/Shaper: differentiates (1x or 2x)

Final amplitude 2-10V



# Fast-Slow Signal Processing

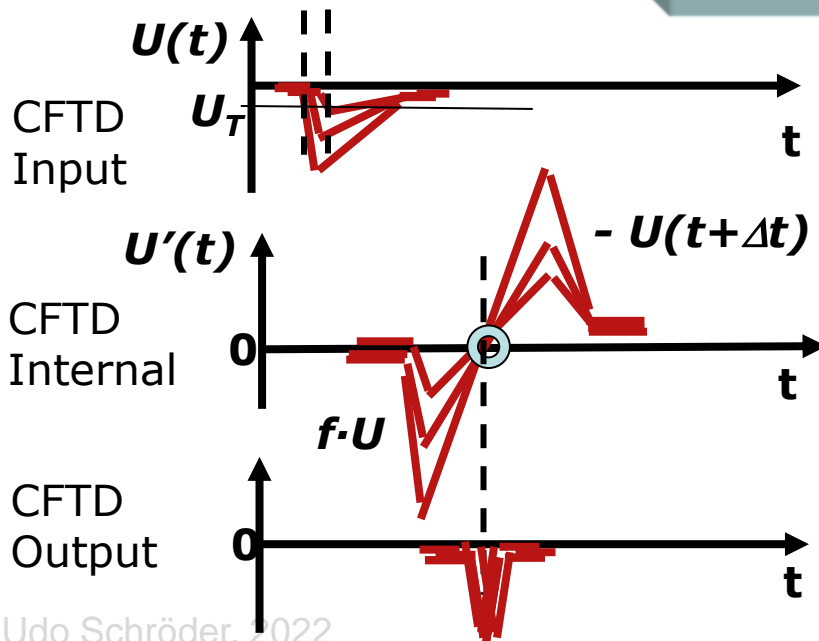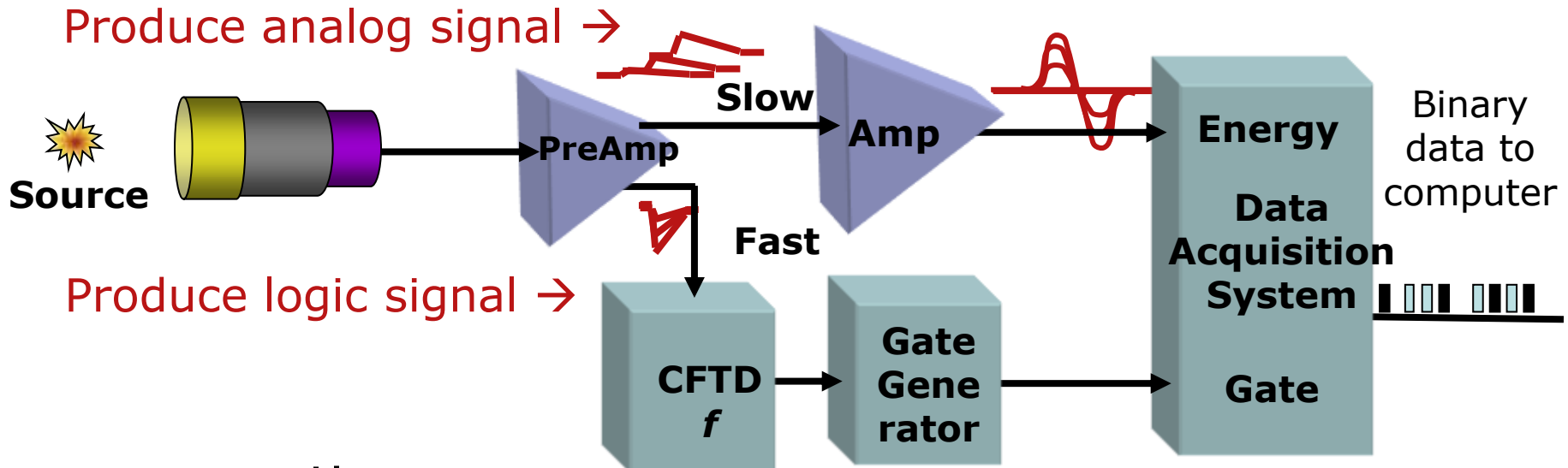

Constant-Fraction Timing Disc.:  
Corrects for "walk"  $t(U)$

$$U'(t) = f \cdot U(t) - U(t+\Delta t)$$


→  $t(U'=0)$  independent of  $U$   
 $t(U'=0) - t(U=U_T)$  measures  $t_R$   
 rise time

(here fraction  $f = 0.5$ )



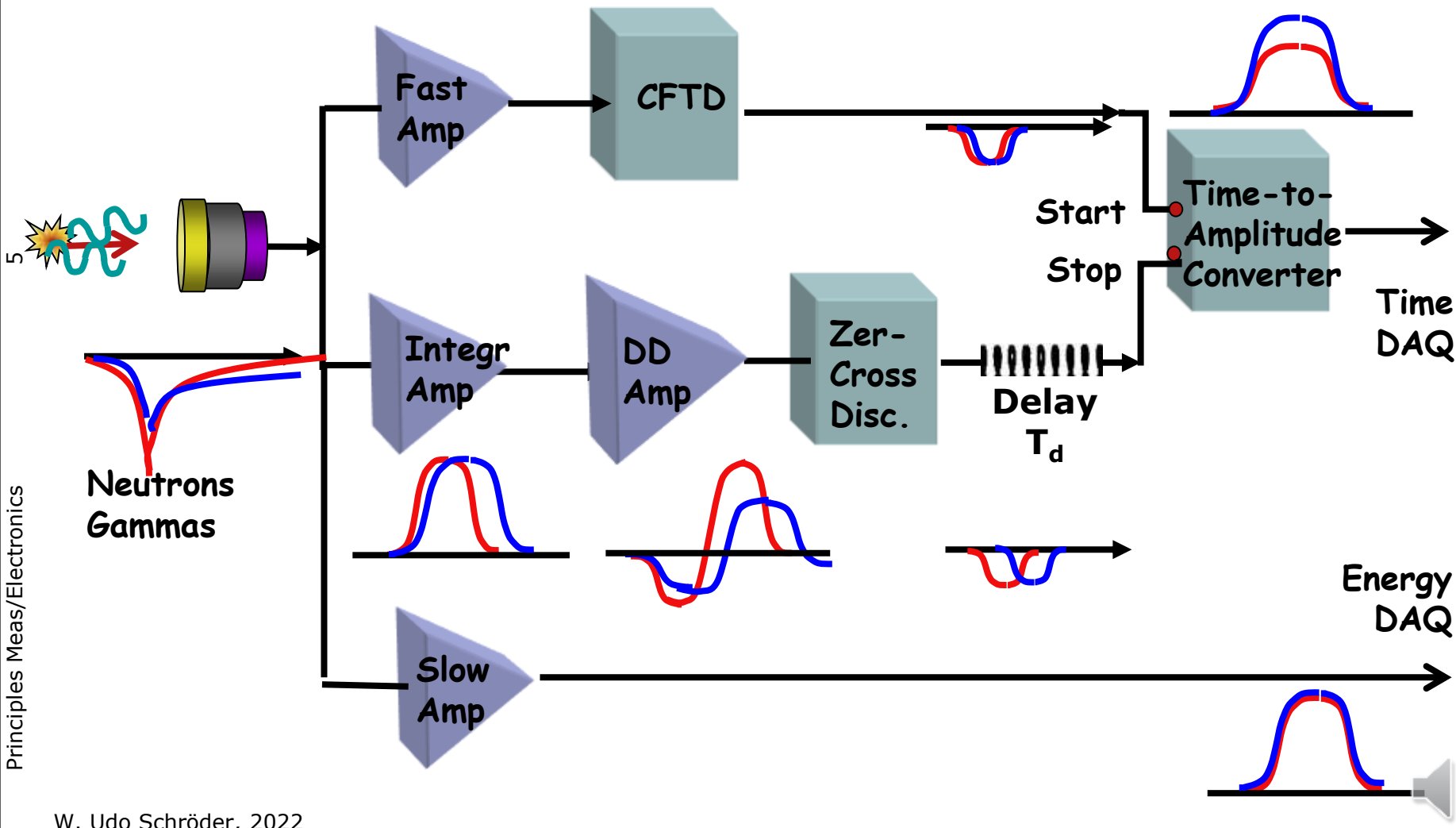
# Pulse Shape Analysis

Different signal decay times for 2 radiation types are translated into different amplitudes


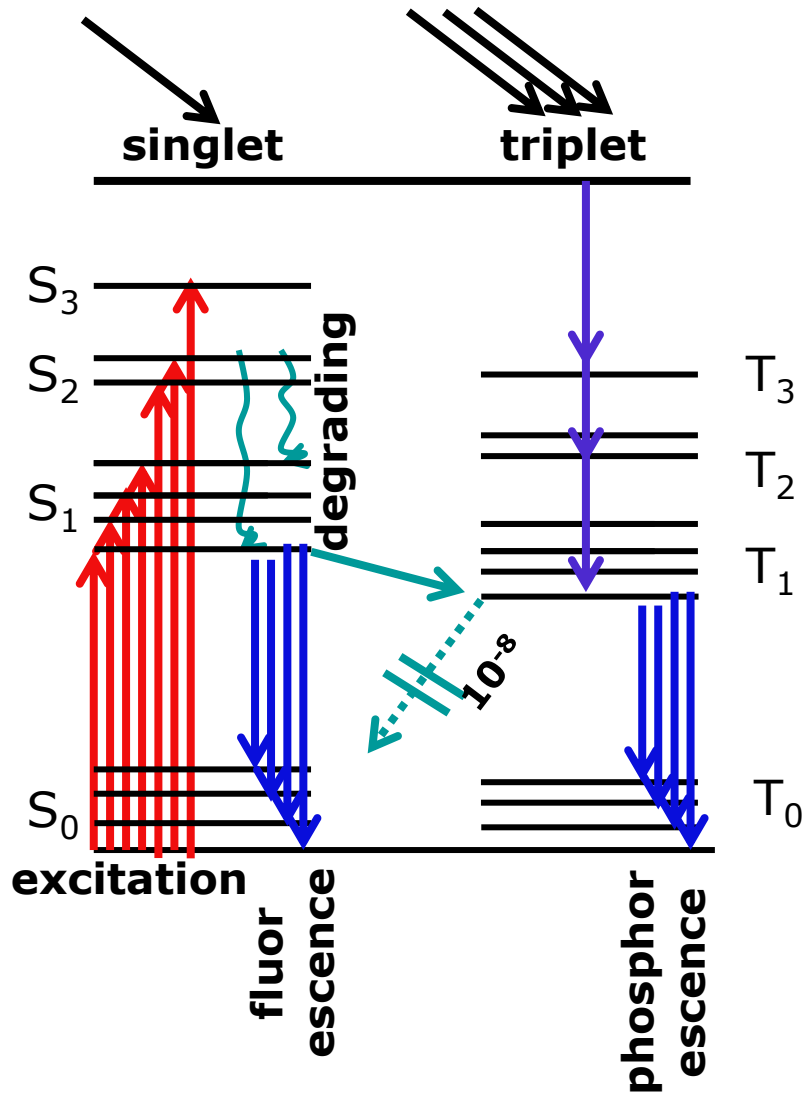
# Scintillation Mechanism: Organic Scintillators



Excitation of molecular states determined by  $\pi$  electrons: singlets ( $^1$ ) and triplets ( $^3$ ). Form vibrational band heads

Trapping of e<sup>-</sup> in triplet states, slow decay to S<sub>0</sub> ground state

Triplet excited (3:1) via ion recombination.

Decay via collisions


**$TT \rightarrow SS + \text{phonons}$**  ( $\tau \sim 300$  ns)

E1 excitation/radiation less transitions depends on ionization density (A,Z,E).

Electromagnetic radiation and heavy particles have different excitation patterns, sequential fluorescence/phosphorescence → PSD discrimination.



# Pulse Shape Analysis

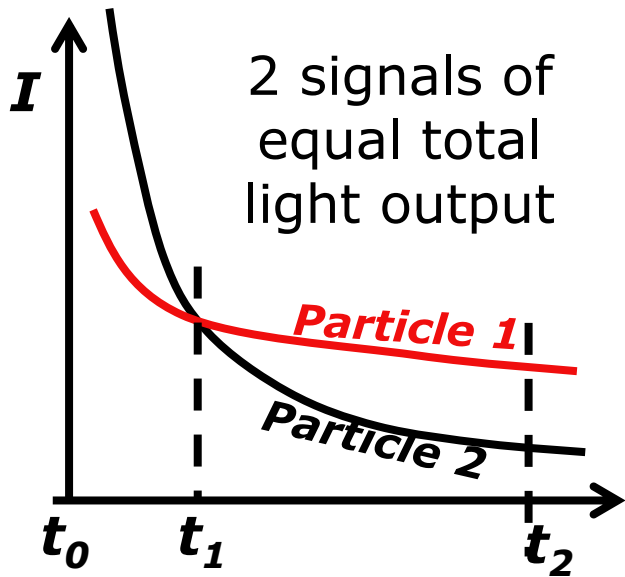



$$Q_1 = \int_{t_0}^{t_1} I(t) dt$$

$$Q_2 = \int_{t_1}^{t_2} I(t) dt$$

$$Q_1 + Q_2 = Q \propto L(\text{Energy})$$




fast  
component  
slow

DISPLAY OUTPUT

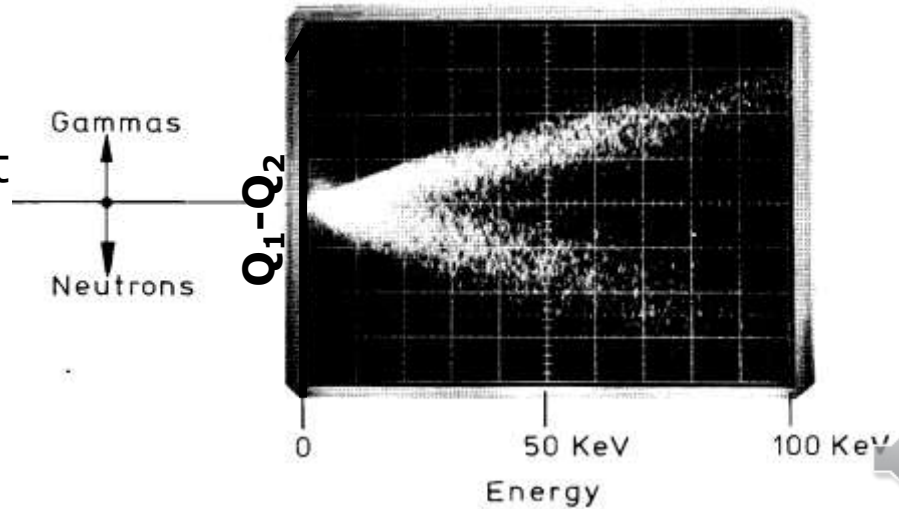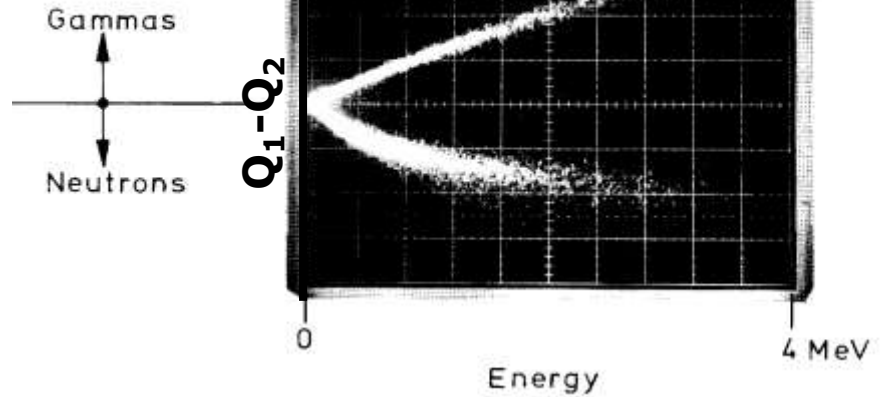
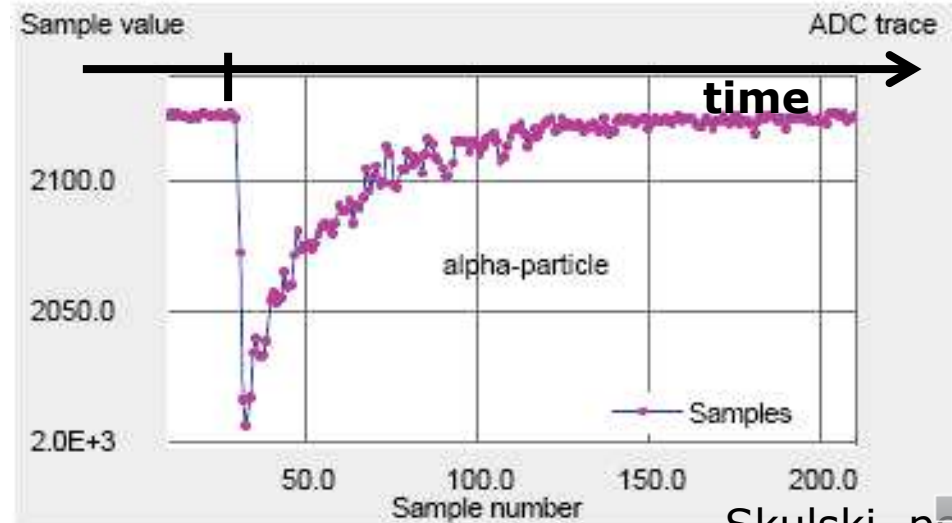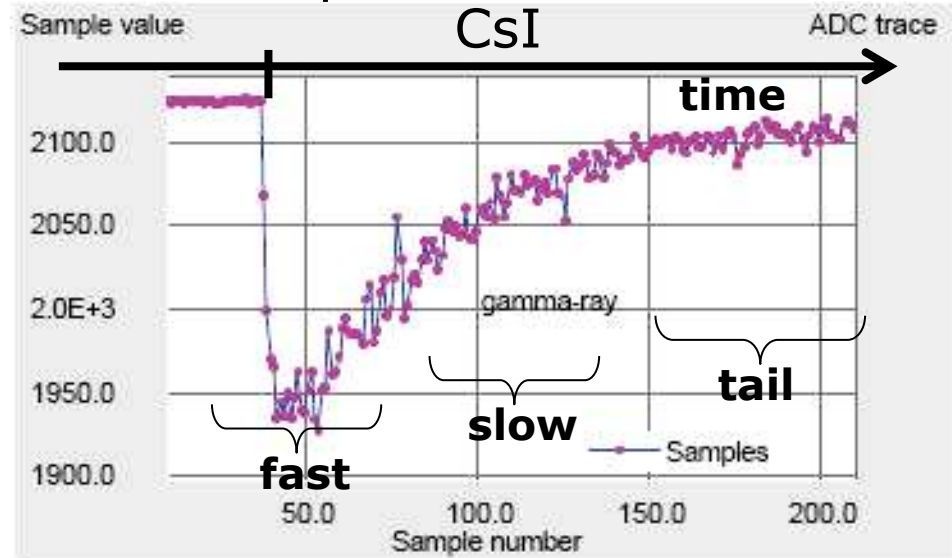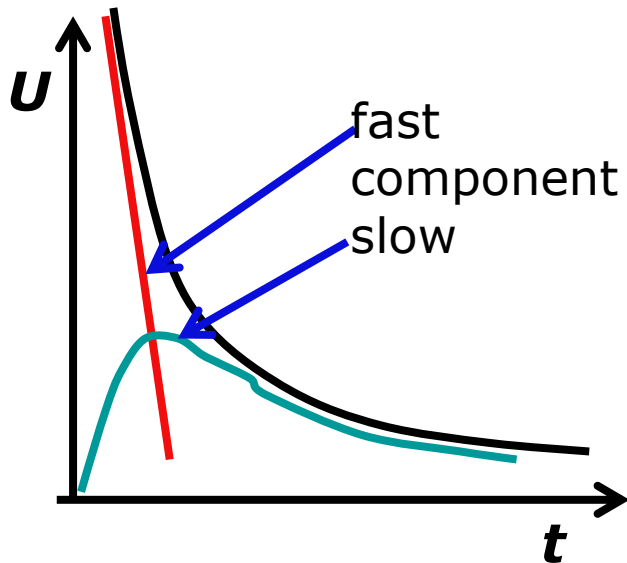
# Radiation Specific Light Output Response

Similar to organic scintillators but not quite as distinct.





Different radiation leads to different mix of fast and slow  $\rightarrow$  ID

**Pulse shape discrimination**

retained electronically  $\rightarrow$



# Non-Linear Light Output Response

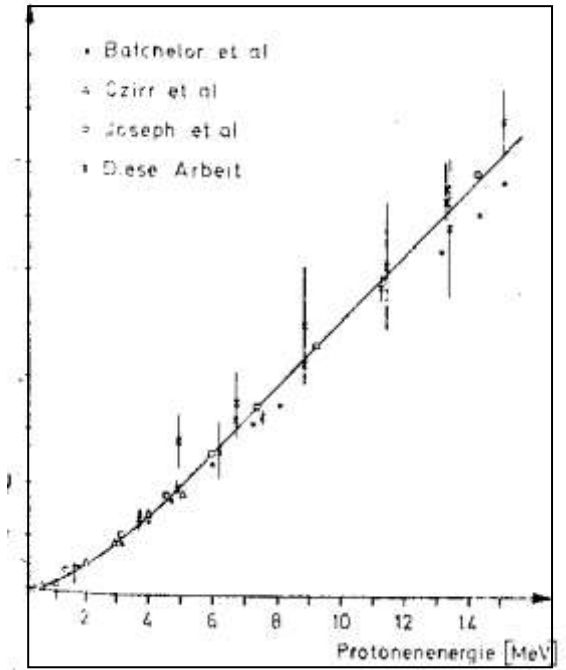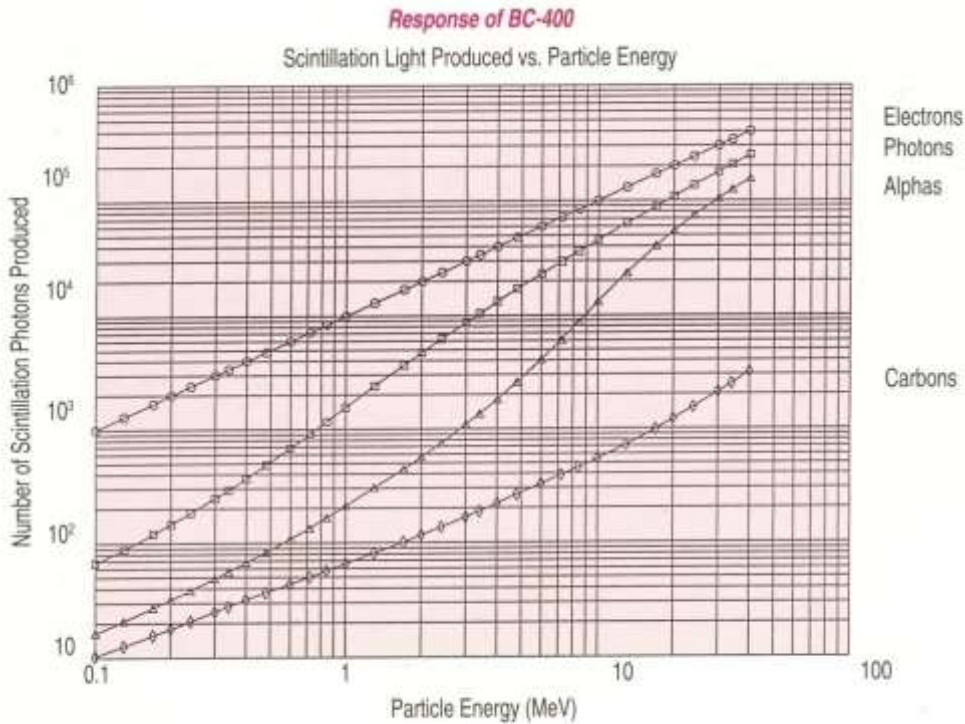

For a given energy, electrons (photons) have the highest light output.

Heavy particles leave weaker useful signals/energy. They are associated with ion recombination/quenching


**NE 213 liquid scintillator:** electron-equivalent ( $ee$ ) and proton recoil energies  $E_e \leftrightarrow E_p$

$$E_e(E_p) = \begin{cases} (0.18 \text{MeV}^{-1/2}) E_p^{3/2} & E_p < 5.25 \text{MeV} \\ 0.63 E_p - 1.10 \text{MeV} & E_p \geq 5.25 \text{MeV} \end{cases}$$

# Efficiency of $p$ -Recoil Neutron Detectors

Angle dependent n-p energy transfer  $\rightarrow$  continuous recoil energy spectrum.

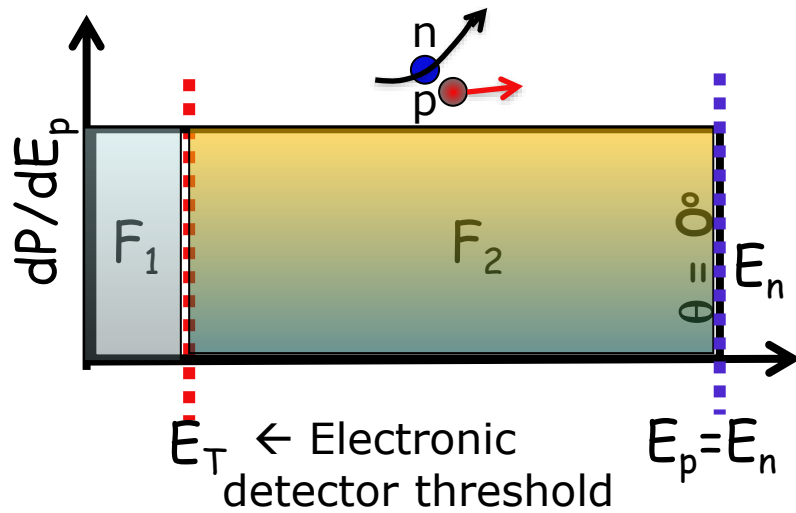
**Idealized proton-recoil energy spectrum  $dP/dE_p$ :**




$$\varepsilon(E_n, E_T) = \frac{F_2}{F_1 + F_2}$$

$$\approx \sigma(E_n) \left[ 1 - \frac{E_T}{E_n} \right]$$
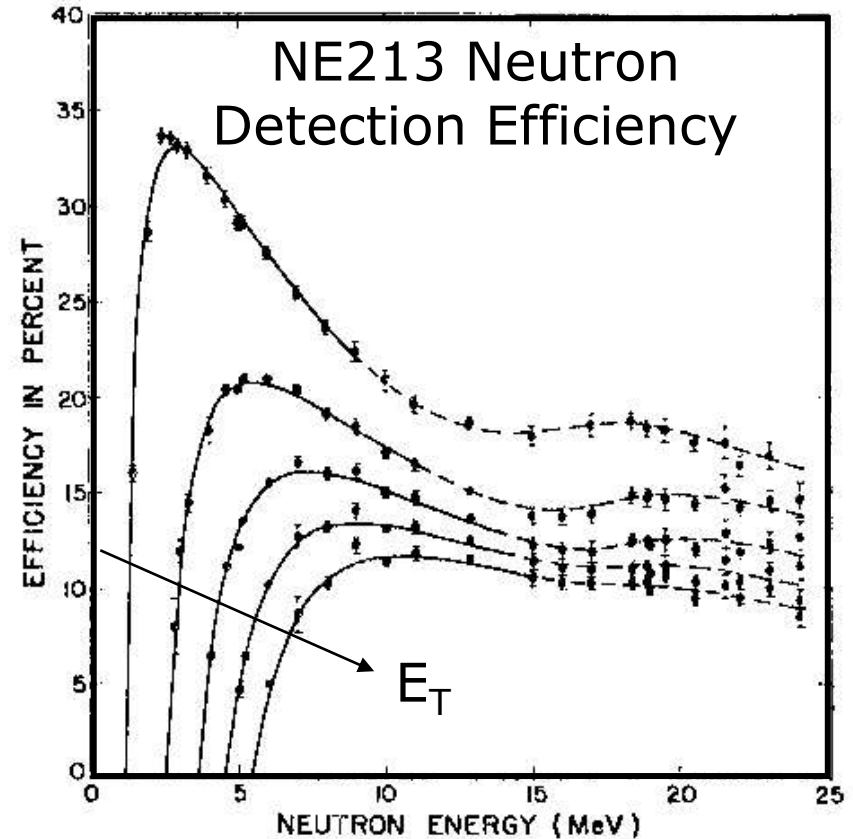
$$\sigma(E_n) = \sum_{X,Y} \sigma_{X(n,Y)}(E_n) \text{ all } n\text{-induced}$$




# Simple Electronics Circuits

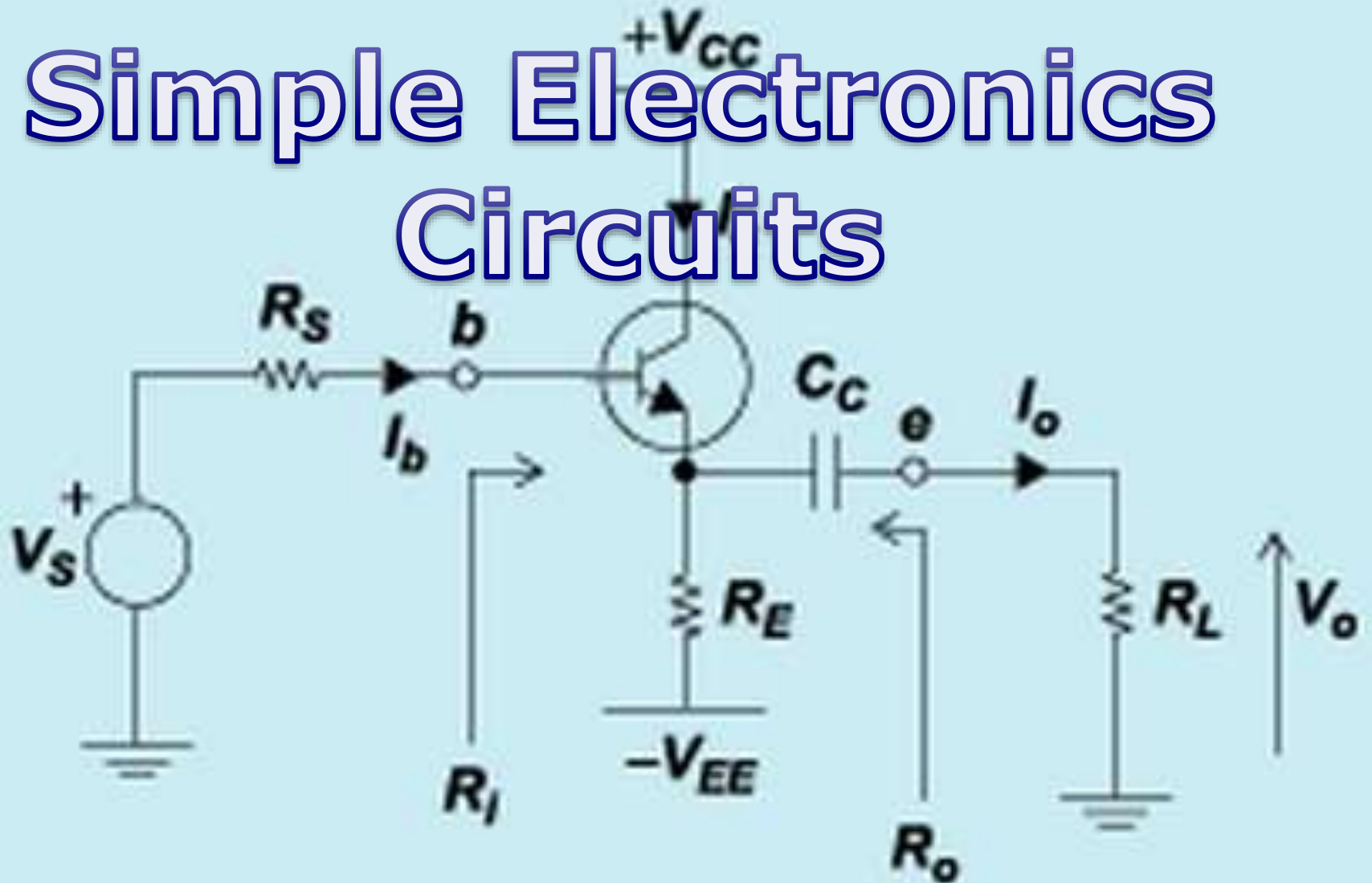


# Transistor Amplifier (Emitter Follower)



Control  
of water  
current

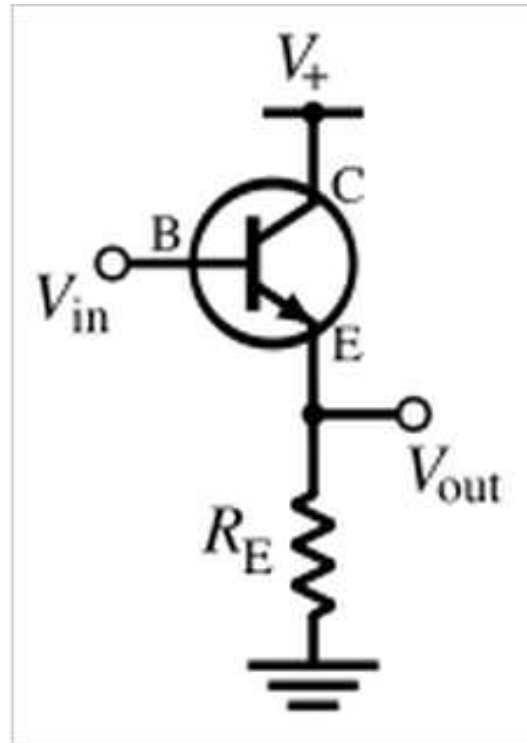

npn transistor

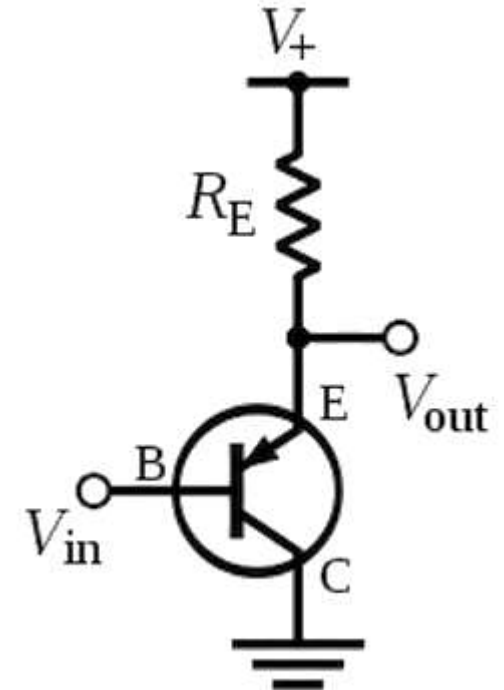

pnp transistor

$$\text{Voltage gain: } A_v = \frac{v_{out}}{v_{in}} \approx 1 \quad \text{current gain} \gg 1$$


# Pre-Amplifiers

**Task:** amplify weak detector signals (mV) to  $\sim 1V$ , transmit through cable.

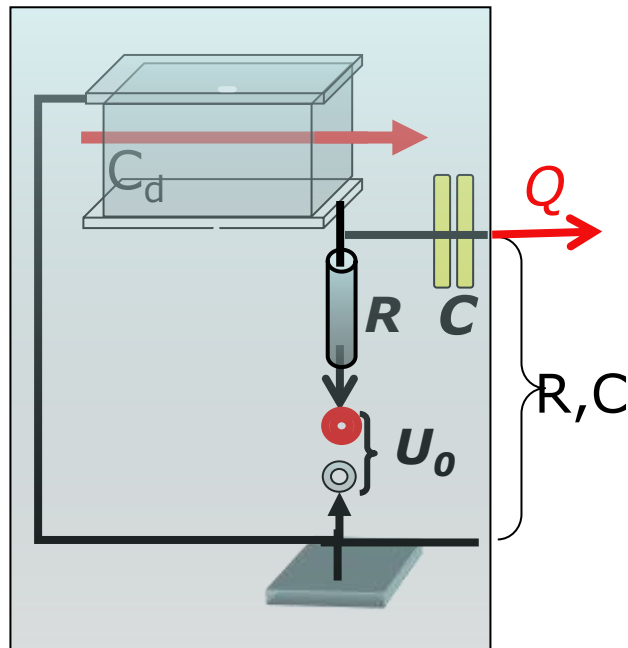**Main types:** **charge-sensitive** or **voltage-sensitive**

Charge sensitive preamps integrate charge  $Q(t) \sim E_{deposit}$  from detector directly. Use for semiconductor diodes.

Voltage sensitive preamps amplify  $U(t) = Q(t)/C$ ,  $C = const.! \rightarrow PM, PC$




Detector is essentially a capacitor  $C_d$ , delivers a time dependent **charge  $Q(t)$**  and **current  $I=dQ/dt$**

For  **$E$**  measurement, integrate  $Q$


For  **$t$**  measurement, differentiate  $Q$

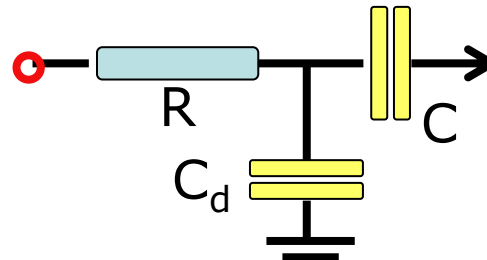Use **operational amplifiers (op-amp)** for either and many other tasks.



Replacement circuit for detector and decoupling

# Operational Amplifiers

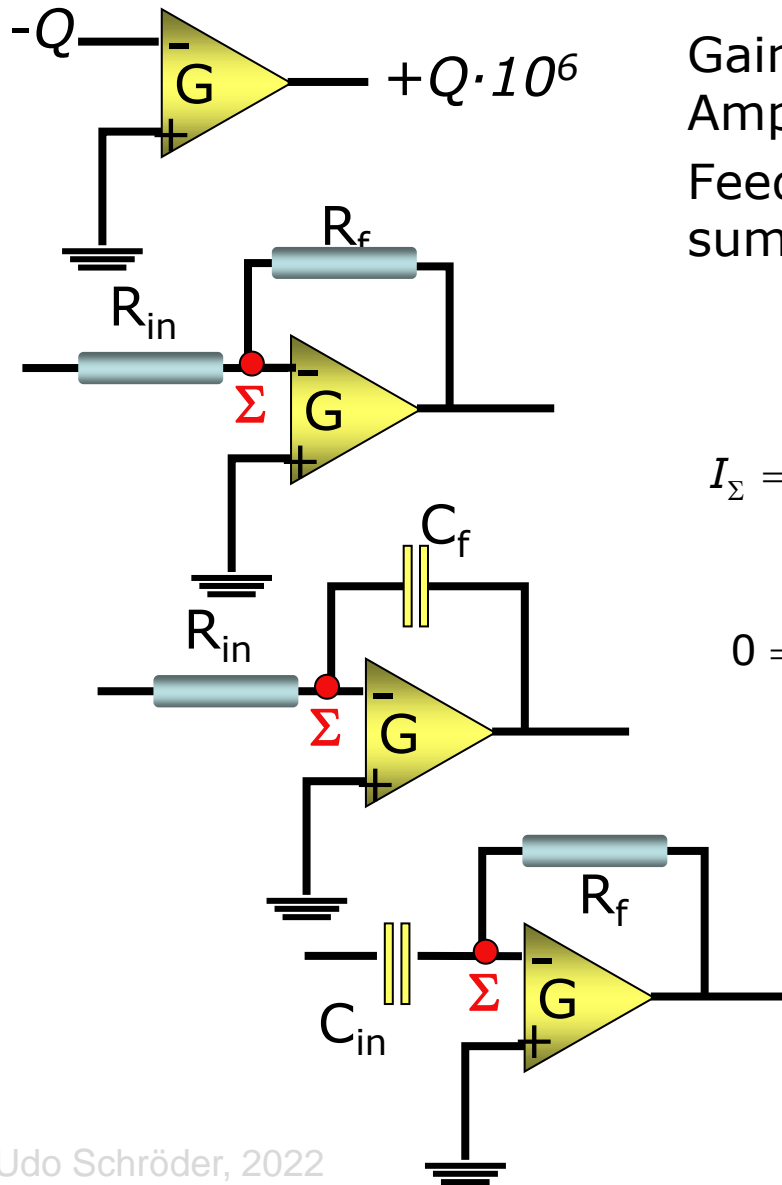

Gain is very high ( $\sim 10^6$ ), inverting.  
 Amp properties determined by feedback c  
 Feeding back negative input signal to the  
 summation point cancels the signal at  $\Sigma$

$$I_{\Sigma} = 0 = I_{in} + I_f = \frac{U_{in}}{R_{in}} + \frac{U_{out}}{R_f} \rightarrow U_{out} = -\frac{R_f}{R_{in}} \cdot U_{in}$$

$$0 = I_{in} + I_f = \frac{U_{in}}{R_{in}} + C_f \frac{dU_{out}}{dt} \rightarrow U_{out} = -\frac{1}{R_{in}C_f} \cdot \int U_{in} dt$$

Integrator


$$U_{out} = -C_{in}R_f \frac{dU_{in}}{dt}$$

Differentiator

# Amplifiers
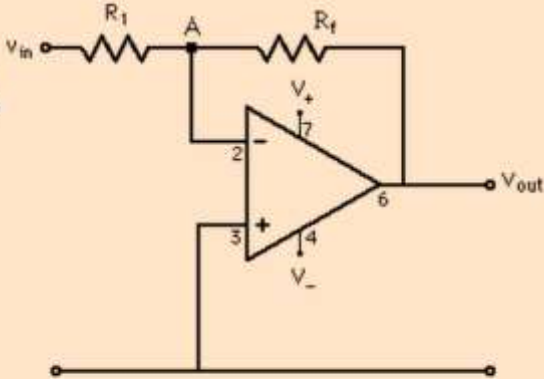
## Inverting Amplifier

The behavior of most configurations of **op-amps** can be determined by applying the "golden rules". For an **inverting amplifier**, the **current rule** tries to drive the current to zero at point A. This requires:




$$\frac{V_{in}}{R_1} = -\frac{V_{out}}{R_f}$$

This gives the voltage amplification

$$\frac{V_{out}}{V_{in}} = -\frac{R_f}{R_1}$$
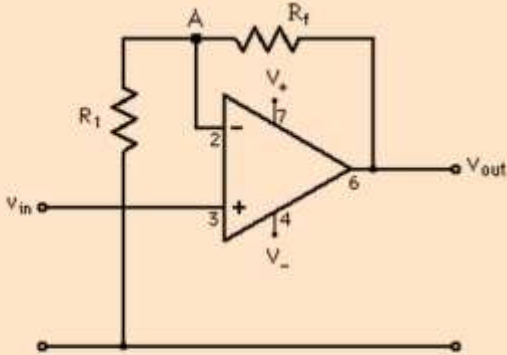
## Non-inverting Amplifier

The behavior of most configurations of **op-amps** can be determined by applying the "golden rules". For an **non-inverting amplifier**, the **current rule** tries to drive the current to zero at point A and the **voltage rule** makes the voltage at A equal to the input voltage. This leads to




$$\frac{V_{in}}{R_1} = \frac{V_{out} - V_{in}}{R_f}$$

and amplification

$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_f}{R_1}$$


# Charge Sensitive Preamp

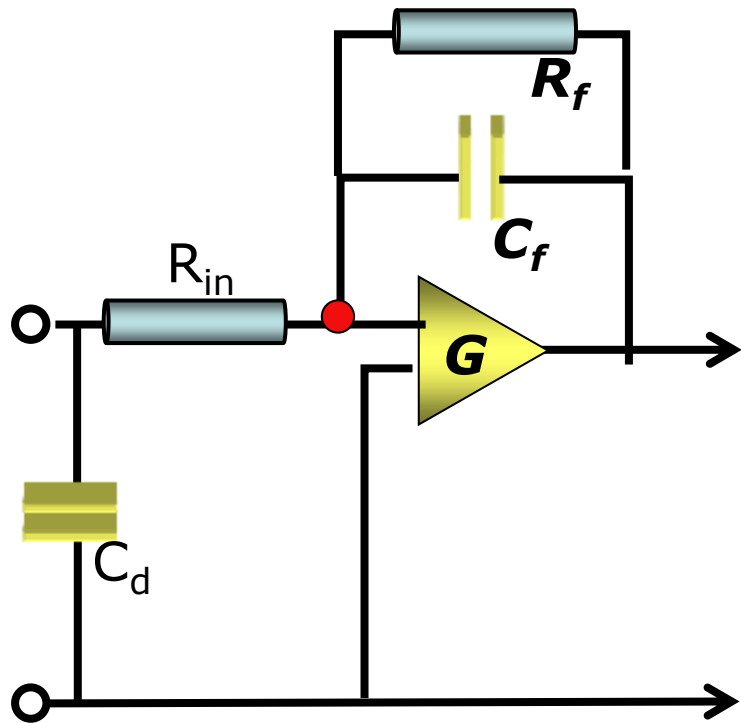

Inverting, integrating preamp

Pulse decay governed by  
 $t_{dec} \approx 1/R_f C_f$ .

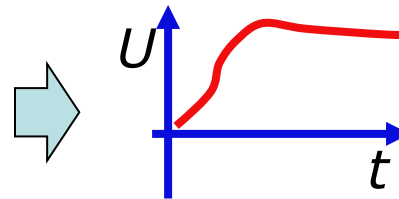
Additional amplifier necessary  
for pulse shaping and gain.






# Main/Shaping Amplifiers

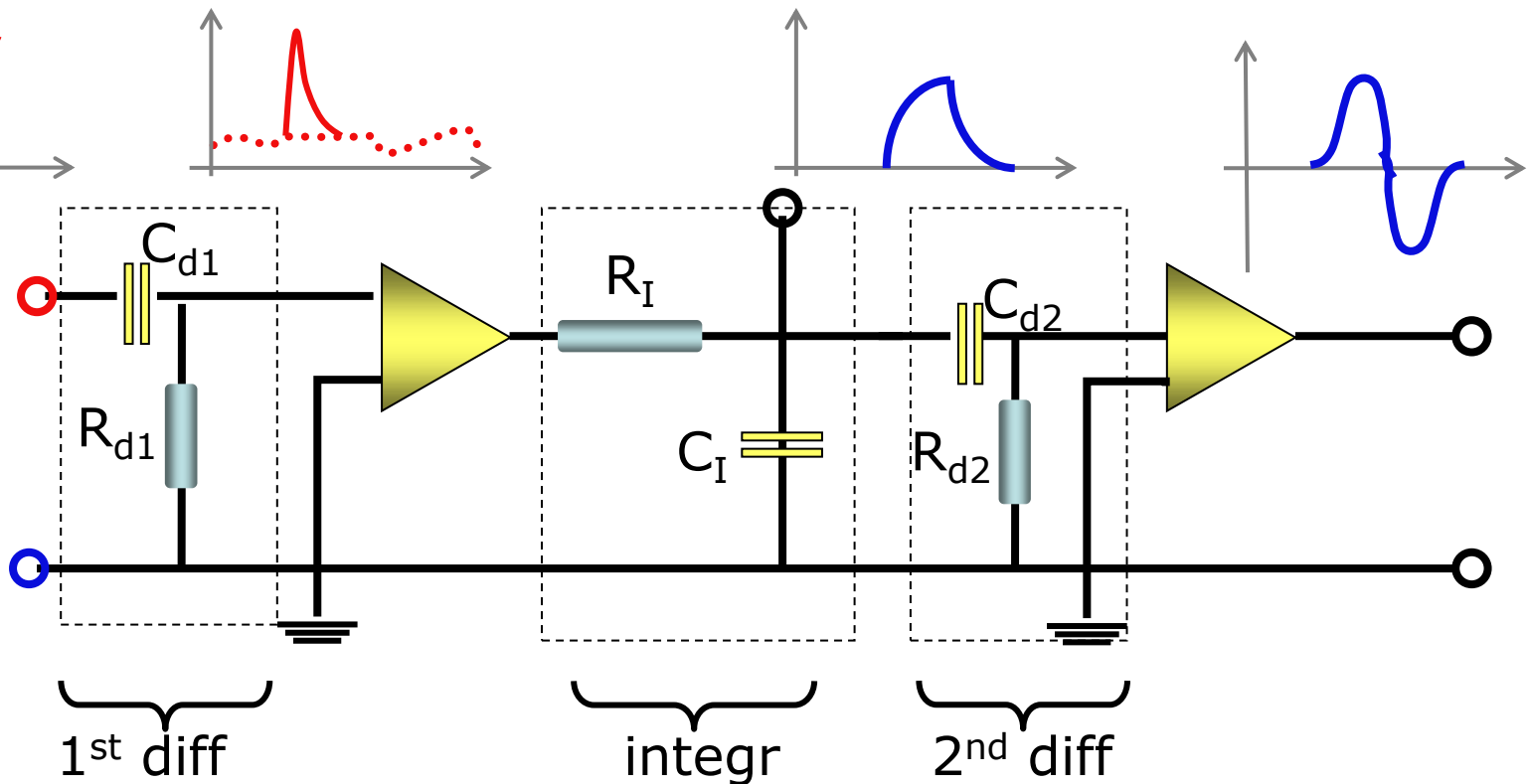- Tasks:
- 1) **Linear** amplification to pulse heights of  $U \approx (1-10)V$
  - 2) Improvement of signal/noise ratio (integration)
  - 3) Pulse shaping (Gaussian shape is best)




# NIM Signal Standards


(National Instruments Methods)

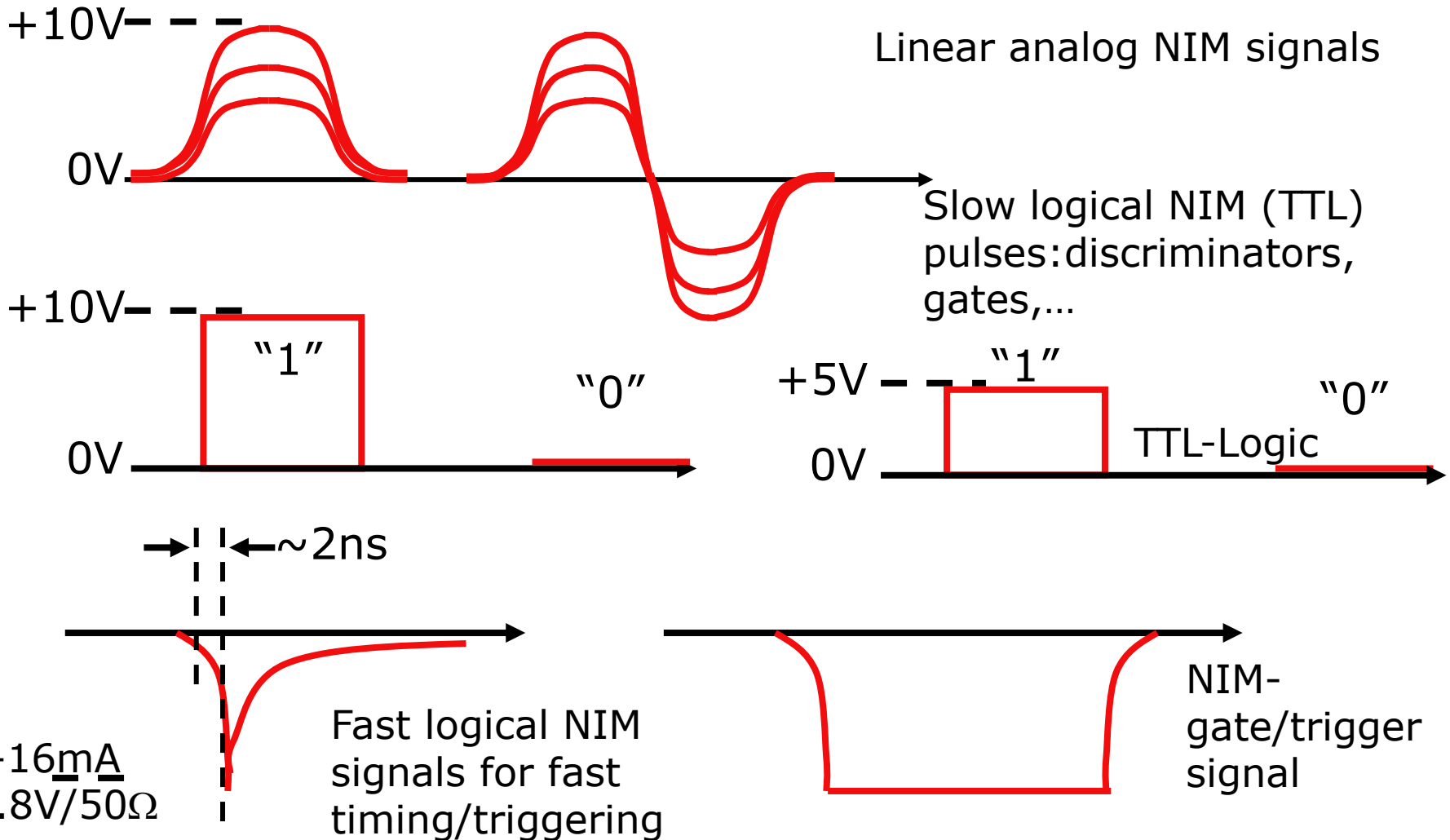

# Discriminator/Trigger

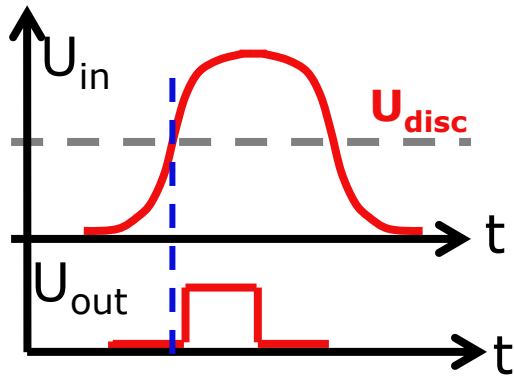


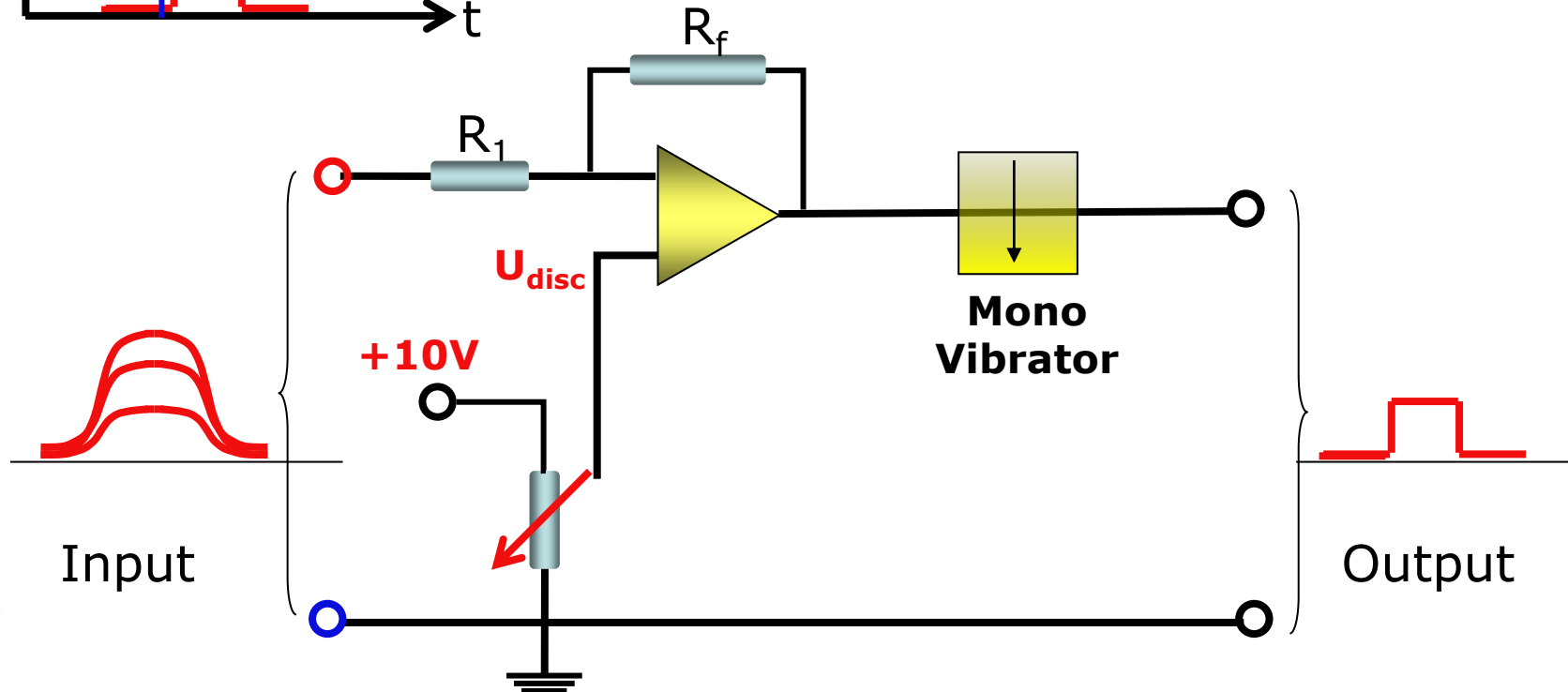**Task:** Produce a logical signal, whenever analog signal exceeds threshold  $U_{disc}$ . Use for logical decisions (open acquisition,...). Exists for slow and fast pulses.



For fast timing, use negative NIM logic units

# Zero-Crossing Triggering

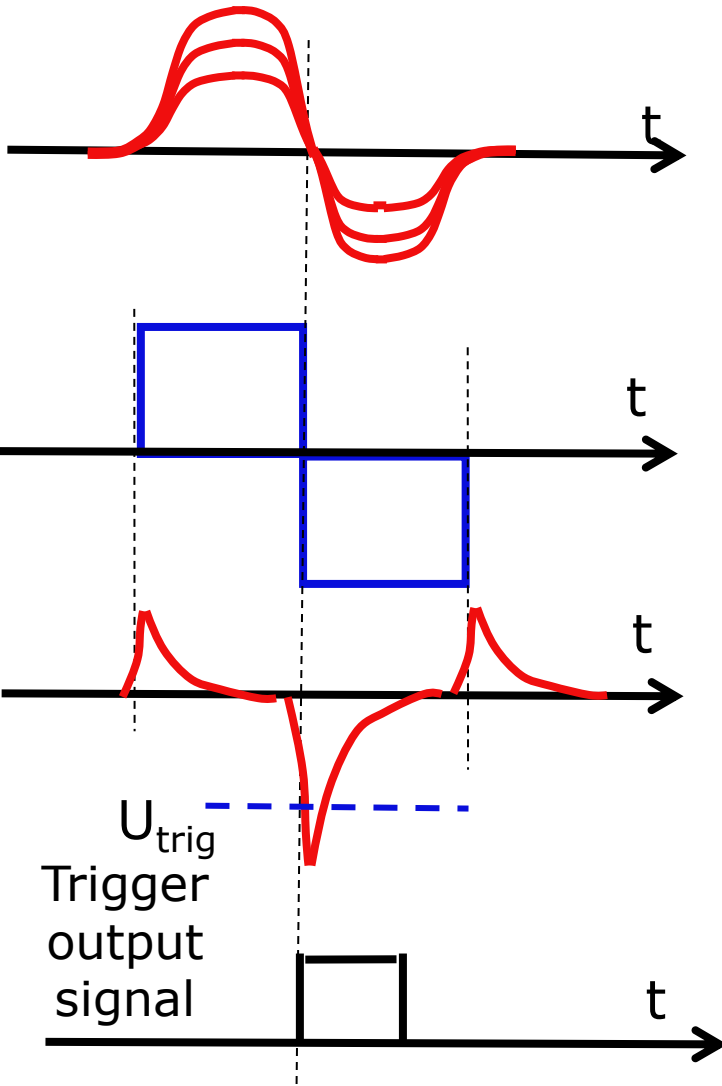

Produce fast, bipolar linear pulse.  
Possible: different gains for positive and negative parts  $\rightarrow$  zero crossing at different time (fraction of time to maximum)


Produce "saturated" uniform pulse

Differentiate saturated pulse, use triplet pulse as input for trigger (negative pulse polarity).

Trigger output appears at zero crossing

(Internal delays neglected)

# Constant-Fraction Discriminator

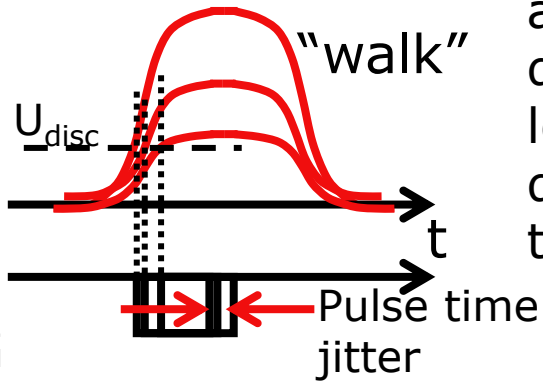


amplitude dependent leading edge discr. output timing

Zero crossing timing always at same physical time, independent of pulse amplitude for fixed pulse shape: no "walk" with energy

21




Principles Meas/Electronics

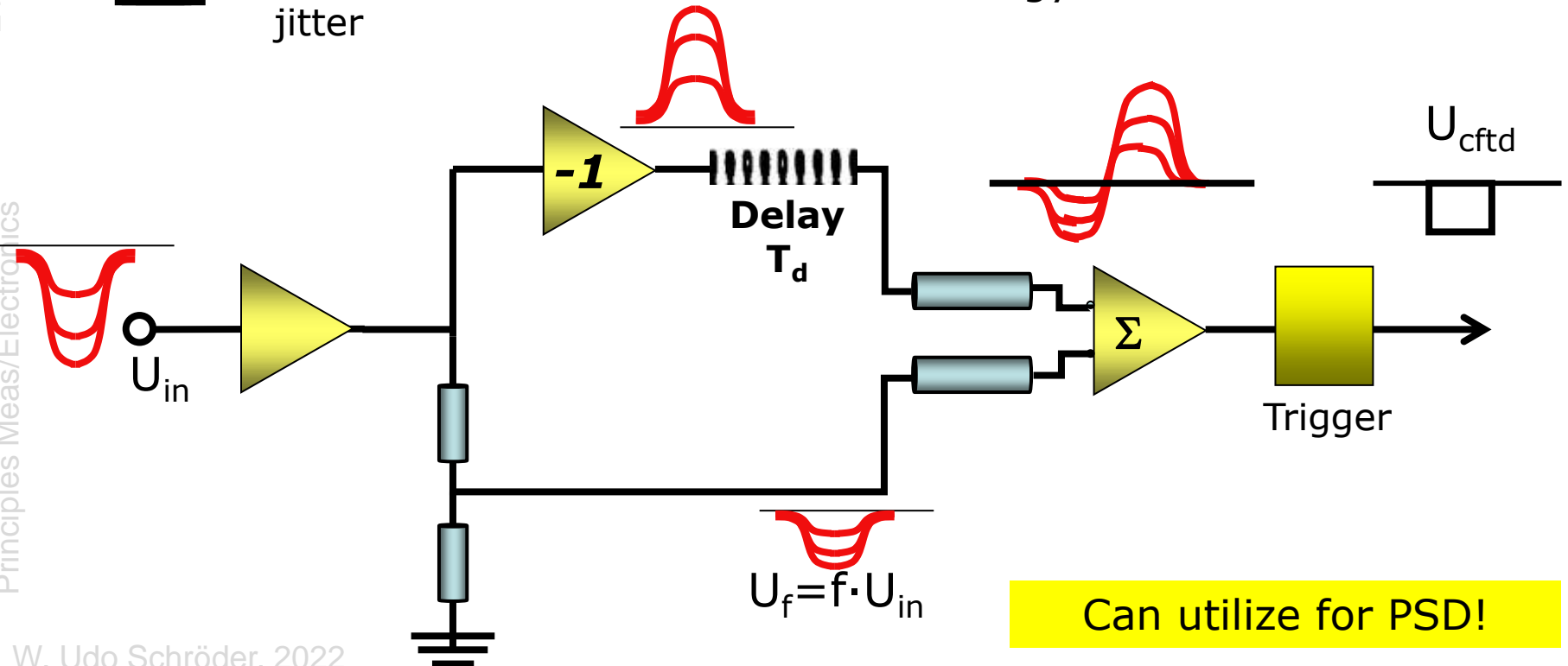



Can utilize for PSD!

# Logic Modules


## Overlap Coincidence

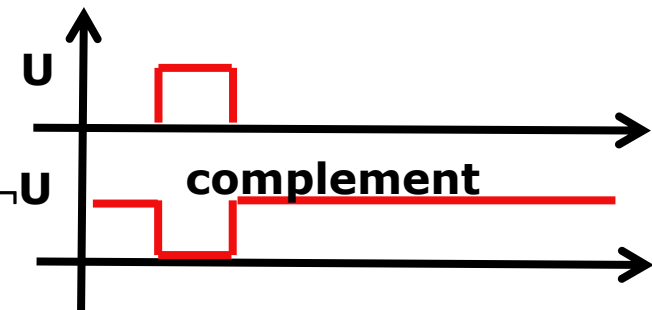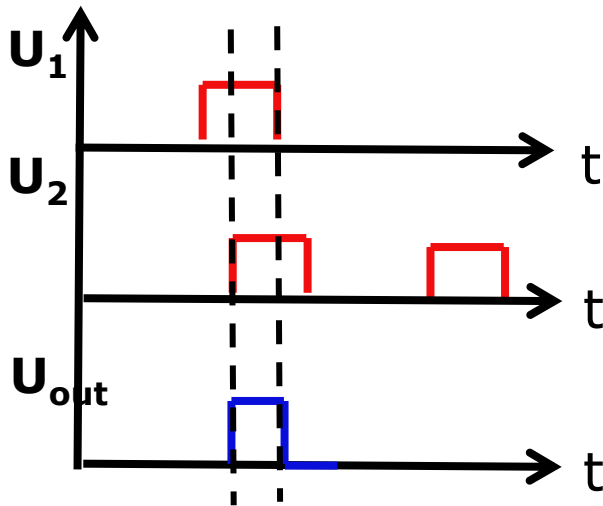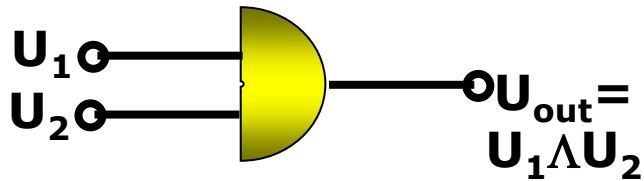

## Or (inclusive)

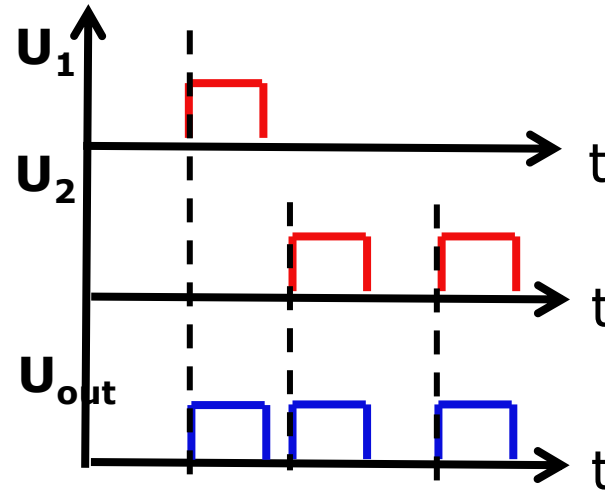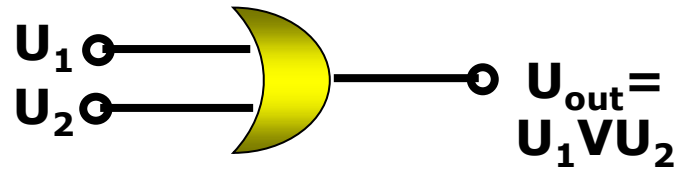

For fast timing: use fast negative logic

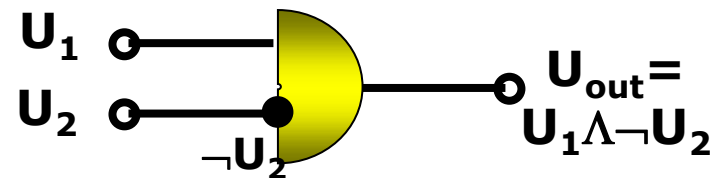

## Anti-Coincidence

# Signal Transmission



Coaxial cables/transmission lines  $\leftrightarrow$  traveling waves in cavity resonators

Wave equation ( $R=0$ ):

$$\frac{\partial^2 U}{\partial z^2} = L \cdot C \cdot \frac{\partial^2 U}{\partial t^2}$$

L: inductivity/length  
C: capacity/length  
depend on diameter  
and dielectric

signal propagation speed  
(speed of light):

$$c = 1/\sqrt{LC}$$

typically  $c^{-1} = 5 \text{ ns/m}$


characteristic resistance  
 $Z_0 = \text{Ohmic resistance!}$

$$Z_0 = \sqrt{L/C}$$


$Z_0 = 50 \Omega$  or  $93 \Omega$   
used for timing,  
spectroscopy, resp.

For  $R \neq 0$ ,  $Z_0(\omega)$  complex


# Impedance Matching

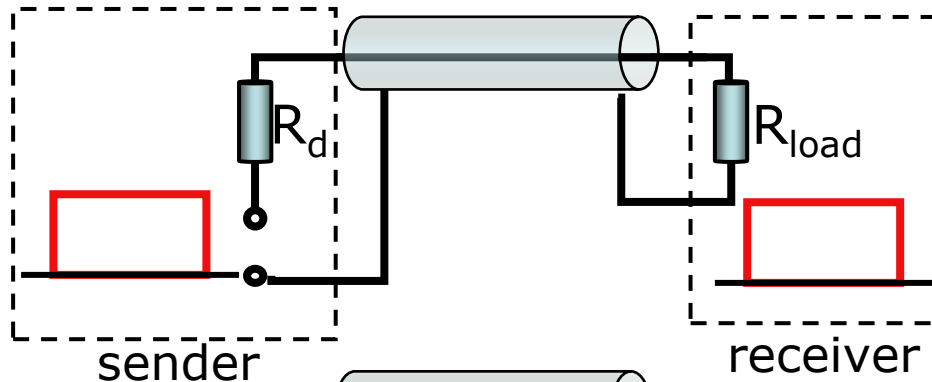

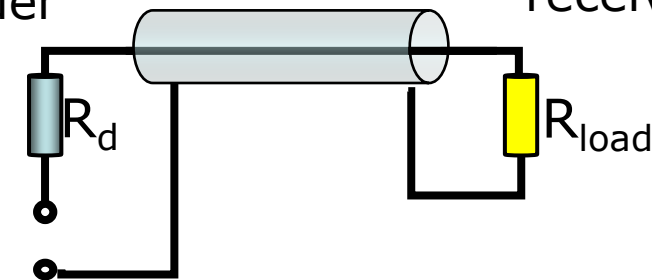For impedance matching,  $R_{load} = Z_0$ , cable looks infinitely long: no reflections from end.



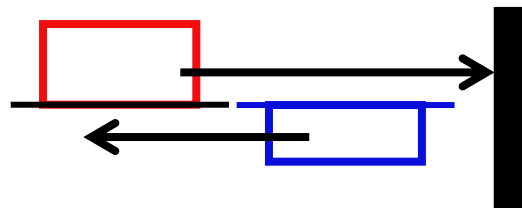For mismatch,  $R_{load} \neq Z_0$ , reflection at end, traveling back, superimpose on signal




$$\frac{U_{refl}}{U_{in}} = \frac{R_{load} - Z_0}{R_{load} + Z_0}$$


Polarity of reflected signal  $R_{load} = 0, \infty$



# Cable Reflections

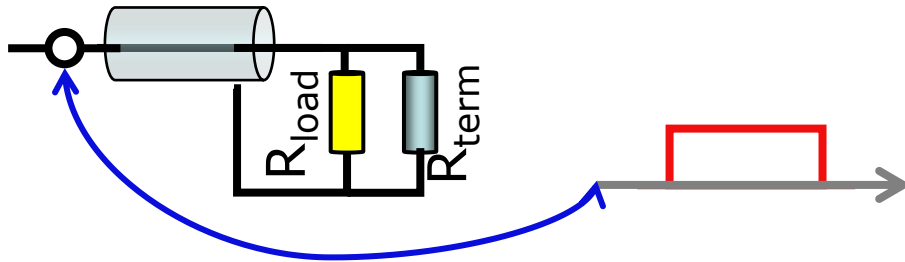


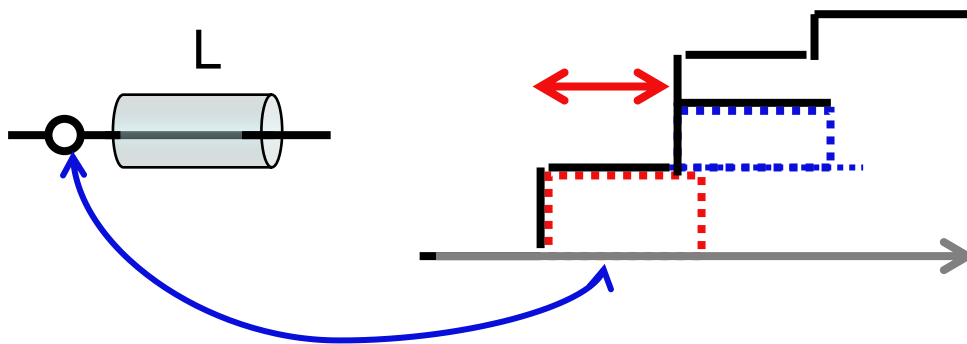Receiver input impedance  $R_{load} \neq Z_0$ ,  $\rightarrow$  use additional Ohmic termination in parallel



Open end:  $R_{load} = \infty$  Input and reflection equal polarity, overlap for  $t > 2T_{cable}$

$$T_{cable} = 2L/c$$

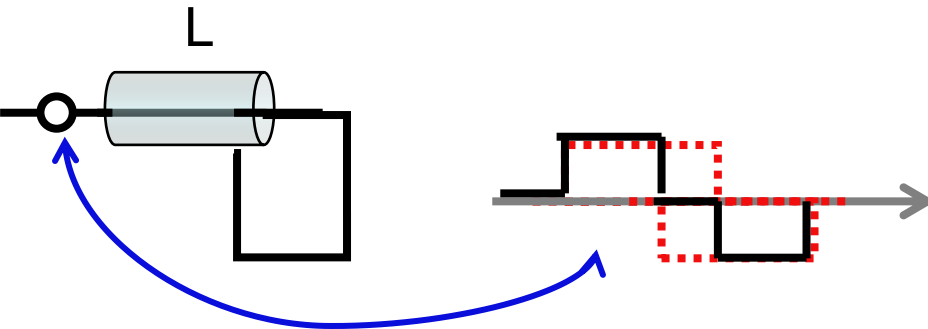

Short:  $R_{load} = 0$ , Input and reflection opposite polarity, superposition = bipolar

Multiple (n) reflections attenuated by  $R^{-n}$



**The End**